

Electricity

Ildikó László, PhD



Dept. Programming Languages and Compilers
Eötvös Loránd University, Budapest, Hungary

Financed from the financial support ELTE won from the Higher Education Restructuring Fund of the Hungarian Government

Capacitance

Capacitors

Electric Current


Electric Current - Ohm's Law

Resistors in Series and Parallel

Capacitors

- ▶ - Capacitor:
 - is a device for storing electric charge;
- ▶ - consists of two conducting objects which do not touch;
- ▶ - typically two parallel plates separated by a distance l , and having an insulator between them;
- ▶ - when connected to a battery, the capacitor becomes charged;
- ▶ - the amount of charge acquired by each plate is:


$$Q = CdV;$$

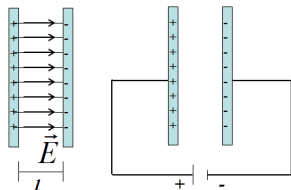

Capacitors

- ▶ - Capacitor:
 - is a device for storing electric charge;
- ▶ - consists of two conducting objects which do not touch;
- ▶ - typically two parallel plates separated by a distance l , and having an insulator between them;
- ▶ - when connected to a battery, the capacitor becomes charged;
- ▶ - the amount of charge acquired by each plate is:


$$Q = CdV;$$

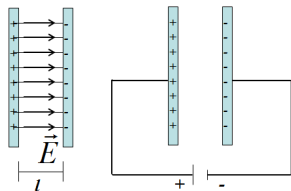

Capacitors

- ▶ - Capacitor:
 - is a device for storing electric charge;
- ▶ - consists of two conducting objects which do not touch;
- ▶ - typically two parallel plates separated by a distance l , and having an insulator between them;
- ▶ - when connected to a battery, the capacitor becomes charged;
- ▶ - the amount of charge acquired by each plate is:


$$Q = CdV;$$

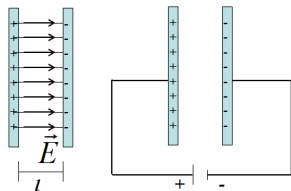

Capacitors

- ▶ - Capacitor:
 - is a device for storing electric charge;
- ▶ - consists of two conducting objects which do not touch;
- ▶ - typically two parallel plates separated by a distance l , and having an insulator between them;
- ▶ - when connected to a battery, the capacitor becomes charged;
- ▶ - the amount of charge acquired by each plate is:


$$Q = CdV;$$

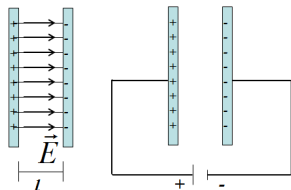

Capacitors

- ▶ - Capacitor:
 - is a device for storing electric charge;
- ▶ - consists of two conducting objects which do not touch;
- ▶ - typically two parallel plates separated by a distance l , and having an insulator between them;
- ▶ - when connected to a battery, the capacitor becomes charged;
- ▶ - the amount of charge acquired by each plate is:

$$Q = CdV;$$

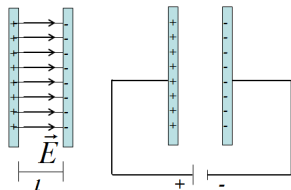

Capacitance

- ▶ - for a parallel plate capacitor of area A we have:

$$\begin{aligned} E &= \frac{Q}{\epsilon_0 A}; \quad dV = - \int_a^b \vec{E} d\vec{l}; \\ C &= \frac{Q}{dV} = \epsilon_0 \frac{A}{l}; \end{aligned} \quad (1)$$

- ▶ - the capacitance of a single isolated conductor,
- for ex. a sphere of radius r ,
relative to $V=0$ at infinity is:

$$\begin{aligned} V &= \frac{1}{4\pi\epsilon_0} \frac{Q}{r}; \\ C &= \frac{Q}{V} = 4\pi\epsilon_0 r; \end{aligned} \quad (2)$$

- ▶ - for a parallel plate capacitor of area A we have:

$$E = \frac{Q}{\epsilon_0 A}; dV = - \int_a^b \vec{E} d\vec{l};$$
$$C = \frac{Q}{dV} = \epsilon_0 \frac{A}{l}; \quad (1)$$

- ▶ - the capacitance of a single isolated conductor,
- for ex. a sphere of radius r ,
relative to $V=0$ at infinity is:

$$V = \frac{1}{4\pi\epsilon_0} \frac{Q}{r};$$
$$C = \frac{Q}{V} = 4\pi\epsilon_0 r; \quad (2)$$

Capacitors in Series and Parallel

- ▶ - if the capacitors are connected in series
 - a charge $+Q$ flows from the battery to the left plate of C_1 ;
 - and $-Q$ flows to the right plate of C_3 ;
- ▶ - if the regions between the capacitors are originally neutral,
 - the net charge there must be zero;
- ▶ - the $+Q$ on C_1 attracts a charge of $-Q$ on the opposite plate - and so on;
- ▶ - a single capacitor that could replace these three in series without affecting the circuit will be:

Capacitors in Series and Parallel

- ▶ - if the capacitors are connected in series
 - a charge $+Q$ flows from the battery to the left plate of C_1 ;
 - and $-Q$ flows to the right plate of C_3 ;
- ▶ - if the regions between the capacitors are originally neutral,
 - the net charge there must be zero;
- ▶ - the $+Q$ on C_1 attracts a charge of $-Q$ on the opposite plate - and so on;
- ▶ - a single capacitor that could replace these three in series without affecting the circuit will be:

Capacitors in Series and Parallel


- ▶ - if the capacitors are connected in series
 - a charge $+Q$ flows from the battery to the left plate of C_1 ;
 - and $-Q$ flows to the right plate of C_3 ;
- ▶ - if the regions between the capacitors are originally neutral,
 - the net charge there must be zero;
- ▶ - the $+Q$ on C_1 attracts a charge of $-Q$ on the opposite plate - and so on;
- ▶ - a single capacitor that could replace these three in series without affecting the circuit will be:

Capacitors in Series and Parallel

- ▶ - if the capacitors are connected in series
 - a charge $+Q$ flows from the battery to the left plate of C_1 ;
 - and $-Q$ flows to the right plate of C_3 ;
- ▶ - if the regions between the capacitors are originally neutral,
 - the net charge there must be zero;
- ▶ - the $+Q$ on C_1 attracts a charge of $-Q$ on the opposite plate - and so on;
- ▶ - a single capacitor that could replace these three in series without affecting the circuit will be:

Capacitors in Series
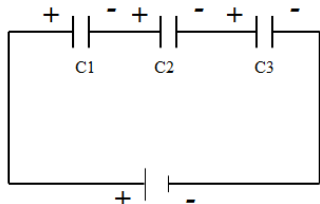
$$\begin{aligned}Q &= CV; V = V_1 + V_2 + V_3; \\Q &= C_i V_i; \frac{Q}{C} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}; \\ \frac{1}{C} &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3};\end{aligned}\tag{3}$$




Capacitors in series

Capacitors in Parallel

- ▶ - if a battery of voltage V is connected to points a ., and b ., we get:
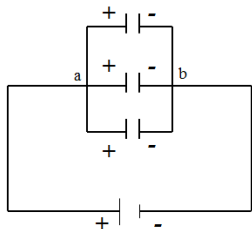
$$\begin{aligned}Q &= Q_1 + Q_2 + Q_3 = C_1 V + C_2 V + C_3 V; \\Q &= CV = C_1 V + C_2 V + C_3 V; \\C &= C_1 + C_2 + C_3;\end{aligned}\tag{4}$$



Capacitors in parallel

Capacitance

Capacitors

Electric Current

Electric Current - Ohm's
Law

Resistors in Series and
Parallel

Capacitance

Capacitors

Electric Current

Electric Current - Ohm's Law

Resistors in Series and Parallel

- ▶ - the electric current in a wire is defined as
- ▶ - the net amount of charge that passes through it at a given point per unit time: $I = \frac{dQ}{dt}$;
- ▶ - in order to produce an electric current in a circuit,
- ▶ - a difference in potential is required;
- ▶ - Ohm established experimentally, that:
 $I \propto V$;
- this is known as Ohm's law;

- ▶ - the electric current in a wire is defined as
- ▶ - the net amount of charge that passes through it at a given point per unit time: $I = \frac{dQ}{dt}$;
- ▶ - in order to produce an electric current in a circuit,
- ▶ - a difference in potential is required;
- ▶ - Ohm established experimentally, that:
 $I \propto V$;
- this is known as Ohm's law;

- ▶ - the electric current in a wire is defined as
- ▶ - the net amount of charge that passes through it at a given point per unit time: $I = \frac{dQ}{dt}$;
- ▶ - in order to produce an electric current in a circuit,
- ▶ - a difference in potential is required;
- ▶ - Ohm established experimentally, that:
 $I \propto V$;
- this is known as Ohm's law;

- ▶ - the electric current in a wire is defined as
- ▶ - the net amount of charge that passes through it at a given point per unit time: $I = \frac{dQ}{dt}$;
- ▶ - in order to produce an electric current in a circuit,
- ▶ - a difference in potential is required;
- ▶ - Ohm established experimentally, that:
 $I \propto V$;
- this is known as Ohm's law;

- ▶ - the electric current in a wire is defined as
- ▶ - the net amount of charge that passes through it at a given point per unit time: $I = \frac{dQ}{dt}$;
- ▶ - in order to produce an electric current in a circuit,
- ▶ - a difference in potential is required;
- ▶ - Ohm established experimentally, that:
 $I \propto V$;
- this is known as Ohm's law;

- ▶ - that is, the current which flows in a metal wire is proportional to the potential difference V applied to its ends;
- ▶ - it depends on the metal wire and is called resistance, R ;
- ▶ - Ohm's law can be written and is known as: $I = \frac{V}{R}$;
- ▶ - the resistance of a uniform metal wire is directly proportional to its length L
- ▶ - and is equal by: $R = \rho \frac{L}{A}$;

- ▶ - that is, the current which flows in a metal wire is proportional to the potential difference V applied to its ends;
- ▶ - it depends on the metal wire and is called resistance, R ;
- ▶ - Ohm's law can be written and is known as: $I = \frac{V}{R}$;
- ▶ - the resistance of a uniform metal wire is directly proportional to its length L
- ▶ - and is equal by: $R = \rho \frac{L}{A}$;

- ▶ - that is, the current which flows in a metal wire is proportional to the potential difference V applied to its ends;
- ▶ - it depends on the metal wire and is called resistance, R ;
- ▶ - Ohm's law can be written and is known as: $I = \frac{V}{R}$;
- ▶ - the resistance of a uniform metal wire is directly proportional to its length L
- ▶ - and is equal by: $R = \rho \frac{L}{A}$;

- ▶ - that is, the current which flows in a metal wire is proportional to the potential difference V applied to its ends;
- ▶ - it depends on the metal wire and is called resistance, R ;
- ▶ - Ohm's law can be written and is known as: $I = \frac{V}{R}$;
- ▶ - the resistance of a uniform metal wire is directly proportional to its length L
- ▶ - and is equal by: $R = \rho \frac{L}{A}$;

- ▶ - that is, the current which flows in a metal wire is proportional to the potential difference V applied to its ends;
- ▶ - it depends on the metal wire and is called resistance, R ;
- ▶ - Ohm's law can be written and is known as: $I = \frac{V}{R}$;
- ▶ - the resistance of a uniform metal wire is directly proportional to its length L
- ▶ - and is equal by: $R = \rho \frac{L}{A}$;

Electric Current and Electric Power

- ▶ - where ρ is the resistivity and depends on the material used and A is the cross section area;
- ▶ - the conductivity of a metal wire is given by: $\sigma = \frac{1}{\rho}$;
- ▶ - the energy transformed when an infinitesimal charge dq moves through a potential difference V is:
 $dU = dqV$;
- ▶ - if dt is the time required for an amount of charge dq to move through a potential difference V
- ▶ - then the power - that is, the rate energy transformed, is: $P = \frac{dU}{dt} = \frac{dq}{dt} V = IV = I(IR) = \frac{V^2}{R}$;

Electric Current and Electric Power

- ▶ - where ρ is the resistivity and depends on the material used and A is the cross section area;
- ▶ - the conductivity of a metal wire is given by: $\sigma = \frac{1}{\rho}$;
- ▶ - the energy transformed when an infinitesimal charge dq moves through a potential difference V is:
 $dU = dqV$;
- ▶ - if dt is the time required for an amount of charge dq to move through a potential difference V
- ▶ - then the power - that is, the rate energy transformed, is: $P = \frac{dU}{dt} = \frac{dq}{dt} V = IV = I(IR) = \frac{V^2}{R}$;

Electric Current and Electric Power

- ▶ - where ρ is the resistivity and depends on the material used and A is the cross section area;
- ▶ - the conductivity of a metal wire is given by: $\sigma = \frac{1}{\rho}$;
- ▶ - the energy transformed when an infinitesimal charge dq moves through a potential difference V is:
 $dU = dqV$;
- ▶ - if dt is the time required for an amount of charge dq to move through a potential difference V
- ▶ - then the power - that is, the rate energy transformed, is: $P = \frac{dU}{dt} = \frac{dq}{dt} V = IV = I(IR) = \frac{V^2}{R}$;

Electric Current and Electric Power

- ▶ - where ρ is the resistivity and depends on the material used and A is the cross section area;
- ▶ - the conductivity of a metal wire is given by: $\sigma = \frac{1}{\rho}$;
- ▶ - the energy transformed when an infinitesimal charge dq moves through a potential difference V is:
 $dU = dqV$;
- ▶ - if dt is the time required for an amount of charge dq to move through a potential difference V
- ▶ - then the power - that is, the rate energy transformed, is: $P = \frac{dU}{dt} = \frac{dq}{dt} V = IV = I(IR) = \frac{V^2}{R}$;

Electric Current and Electric Power

- ▶ - where ρ is the resistivity and depends on the material used and A is the cross section area;
- ▶ - the conductivity of a metal wire is given by: $\sigma = \frac{1}{\rho}$;
- ▶ - the energy transformed when an infinitesimal charge dq moves through a potential difference V is:
 $dU = dqV$;
- ▶ - if dt is the time required for an amount of charge dq to move through a potential difference V
- ▶ - then the power - that is, the rate energy transformed, is: $P = \frac{dU}{dt} = \frac{dq}{dt} V = IV = I(IR) = \frac{V^2}{R}$;

Capacitance

Capacitors

Electric Current

Electric Current - Ohm's
Law

Resistors in Series and
Parallel

Capacitance

Capacitors


Electric Current

Electric Current - Ohm's Law

Resistors in Series and Parallel


Resistors in Series

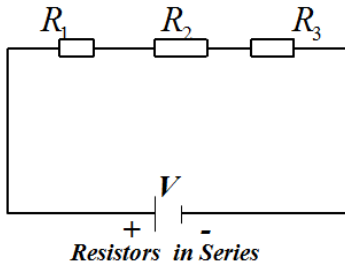- ▶ - when two or more resistors are connected so that the same current passes through each of them, (see fig.)
- ▶ - they are said to be connected in series;
- ▶ - if the voltage applied is V , then from Ohm's law for an equivalent single resistor R , we have: $R = \frac{V}{I}$;




Resistors in Series

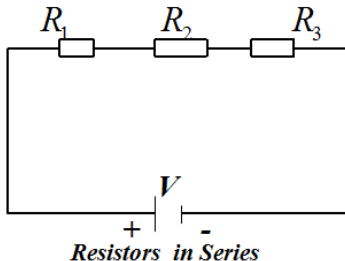- ▶ - when two or more resistors are connected so that the same current passes through each of them, (see fig.)
- ▶ - they are said to be connected in series;
- ▶ - if the voltage applied is V , then from Ohm's law for an equivalent single resistor R , we have: $R = \frac{V}{I}$;



Resistors in Series

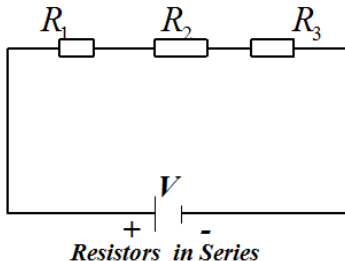- ▶ - when two or more resistors are connected so that the same current passes through each of them, (see fig.)
- ▶ - they are said to be connected in series;
- ▶ - if the voltage applied is V , then from Ohm's law for an equivalent single resistor R , we have: $R = \frac{V}{I}$;



Resistors in Series

- ▶ - because of conservation energy, the total voltage is equal to the sum of the voltages on each resistor;
- ▶ - that is: $V = V_1 + V_2 + V_3$;
- where V_i is the potential difference across each resistor;
- ▶ - from where we get: $R = R_1 + R_2 + R_3$;

Resistors in Series


- ▶ - because of conservation energy, the total voltage is equal to the sum of the voltages on each resistor;
- ▶ - that is: $V = V_1 + V_2 + V_3$;
- where V_i is the potential difference across each resistor;
- ▶ - from where we get: $R = R_1 + R_2 + R_3$;

Resistors in Series

- ▶ - because of conservation energy, the total voltage is equal to the sum of the voltages on each resistor;
- ▶ - that is: $V = V_1 + V_2 + V_3$;
- where V_i is the potential difference across each resistor;
- ▶ - from where we get: $R = R_1 + R_2 + R_3$;

Kirchhoff's first or Junction Rule

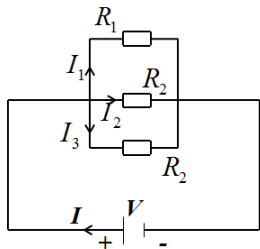
- ▶ - at any junction point, the sum of all currents entering the junction, must equal the sum of all currents leaving the junction;
- ▶ - that is: $I = I_1 + I_2 + I_3$;



Kirchhoff's first or Junction Rule

Kirchhoff's first or Junction Rule

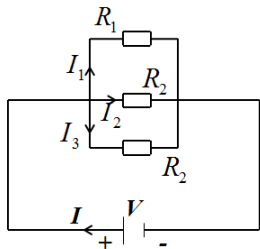- ▶ - at any junction point, the sum of all currents entering the junction, must equal the sum of all currents leaving the junction;
- ▶ - that is: $I = I_1 + I_2 + I_3$;




Kirchhoff's first or Junction Rule

Resistors in Parallel

- ▶ - when two or more resistors are connected in parallel, the voltage on each resistor will be the same;
- ▶ - from Ohm's law we have:
$$I_1 = \frac{V}{R_1}, \quad I_2 = \frac{V}{R_2}, \quad I_3 = \frac{V}{R_3};$$
- ▶ - using Kirchhoff's first or Junction Rule for the equivalent single resistor R we get:
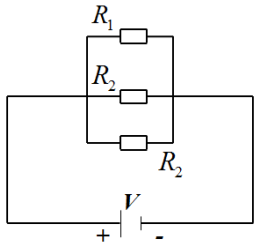
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3};$$



Resistors in Parallel

Resistors in Parallel


- ▶ - when two or more resistors are connected in parallel, the voltage on each resistor will be the same;

- ▶ - from Ohm's law we have:

$$I_1 = \frac{V}{R_1}, \quad I_2 = \frac{V}{R_2}, \quad I_3 = \frac{V}{R_3};$$

- ▶ - using Kirchhoff's first or Junction Rule for the equivalent single resistor R we get:
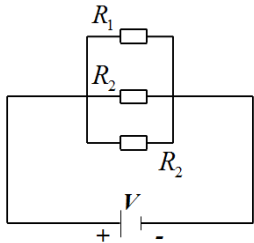
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3};$$




Resistors in Parallel

Resistors in Parallel

- ▶ - when two or more resistors are connected in parallel, the voltage on each resistor will be the same;
- ▶ - from Ohm's law we have:
$$I_1 = \frac{V}{R_1}, \quad I_2 = \frac{V}{R_2}, \quad I_3 = \frac{V}{R_3};$$
- ▶ - using Kirchhoff's first or Junction Rule for the equivalent single resistor R we get:
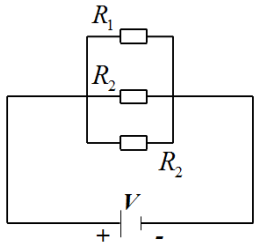
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3};$$



Resistors in Parallel